Static Electricity and Simple Circuits

Grade 3 Science Worksheet - Challenge Me

Name _____ Date _____

Write yes or no.

1. A loop has a battery, a bulb and a paper clip joining a gap in the wire. Does the bulb light? Answer: _____

2. A loop has a battery, a bulb and a wooden stick across a gap. Does the bulb light? Answer: _____

3. A battery is joined to a bulb in a closed loop, and a switch in the loop is closed. Does the bulb light? Answer: _____

4. A loop has a battery, a bulb and a copper coin joining a gap in the wire. Does the bulb light? Answer: _____

5. A loop has a battery, a bulb and a plastic spoon joining a gap in the wire. Does the bulb light? Answer: _____

6. A loop has a battery, a bulb and a glass marble joining a gap in the wire. Does the bulb light? Answer: _____

7. A loop has a battery, a bulb and a rubber band joining a gap in the wire. Does the bulb light? Answer: _____

8. A loop has a battery, a bulb and a metal key that touches both ends of the gap. Does the bulb light? Answer: _____

Scan to get this marked free. No screen time for your child.
Print it · do it in pencil · scan it · PencilGo picks the next sheet.

Static Electricity and Simple Circuits

Answer Key - Grade 3 Science Worksheet - Challenge Me

Write yes or no.

1. A loop has a battery, a bulb and a paper clip joining a gap in the wire. Does the bulb light? Answer: **yes**

2. A loop has a battery, a bulb and a wooden stick across a gap. Does the bulb light? Answer: **no**

3. A battery is joined to a bulb in a closed loop, and a switch in the loop is closed. Does the bulb light? Answer: **yes**

4. A loop has a battery, a bulb and a copper coin joining a gap in the wire. Does the bulb light? Answer: **yes**

5. A loop has a battery, a bulb and a plastic spoon joining a gap in the wire. Does the bulb light? Answer: **no**

6. A loop has a battery, a bulb and a glass marble joining a gap in the wire. Does the bulb light? Answer: **no**

7. A loop has a battery, a bulb and a rubber band joining a gap in the wire. Does the bulb light? Answer: **no**

8. A loop has a battery, a bulb and a metal key that touches both ends of the gap. Does the bulb light? Answer: **yes**